

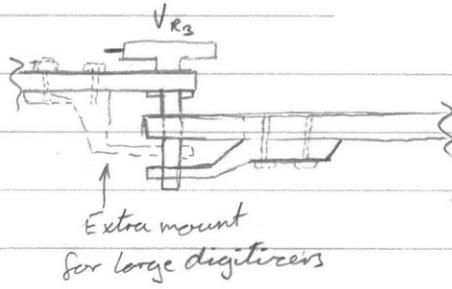


Base

Middle


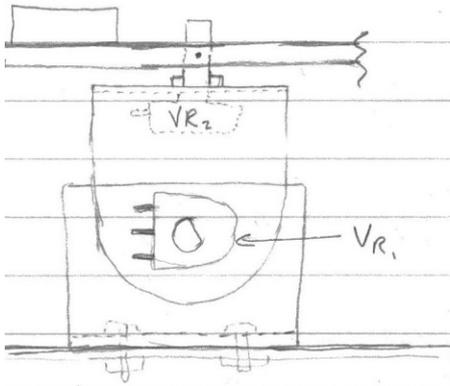


Box (bolted to board)

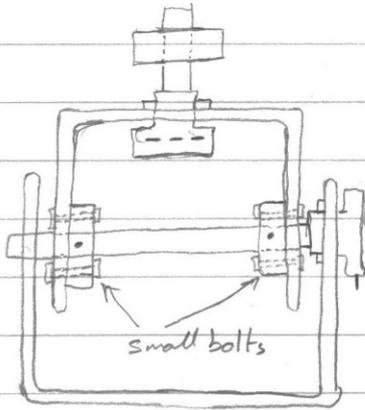


End (Version 1)


End (Version 2)

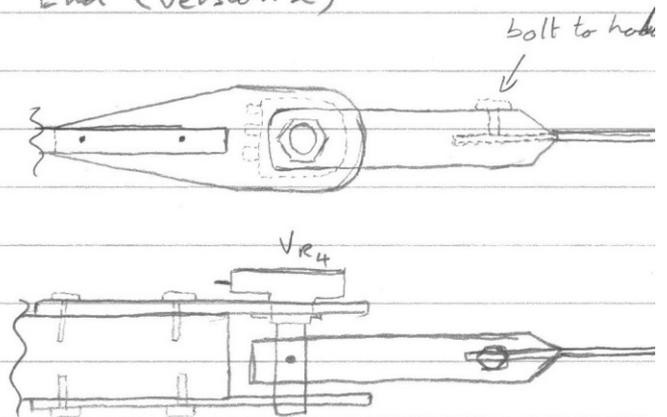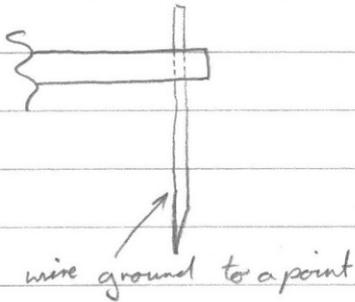

The exact sizes and design will depend on the parts available.

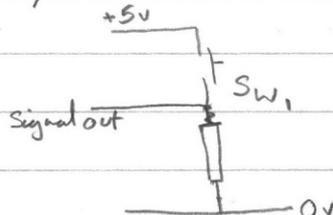Optionally include a push-switch somewhere with the circuit



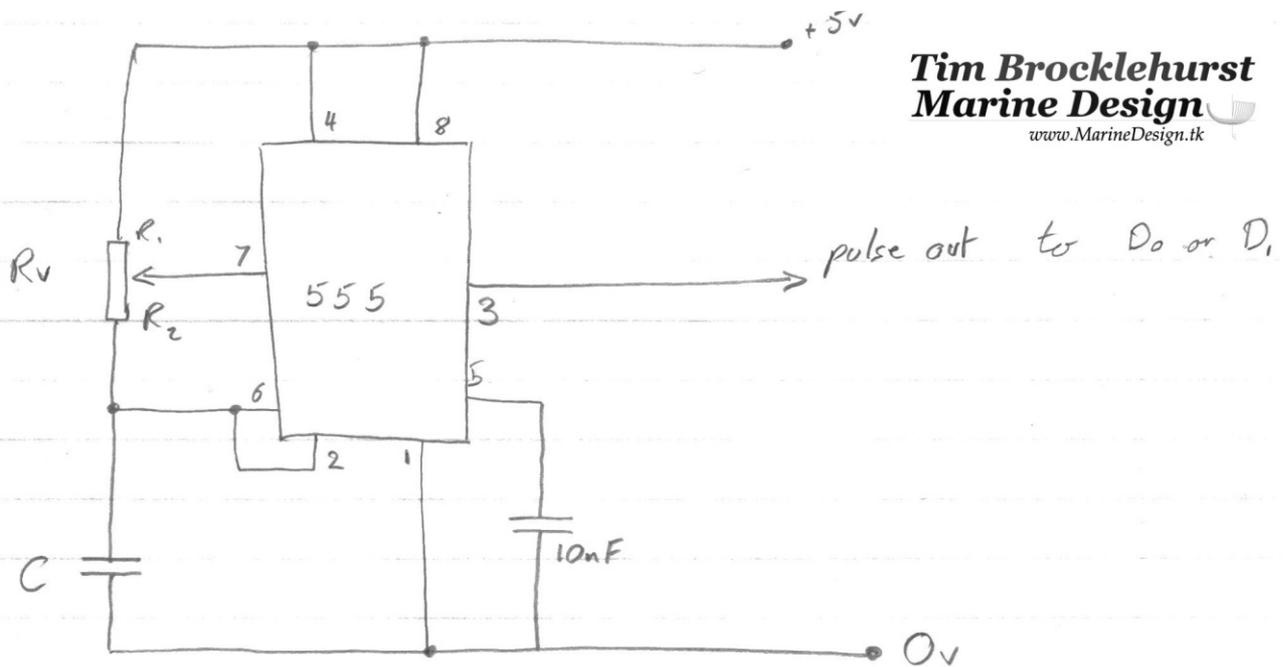

$$f = \frac{1.44}{(R_1 + 2R_2) \times C}$$

$$\text{High time} = 0.69 (R_1 + R_2) \times C$$

$$\text{Low time} = 0.69 (R_2 \times C)$$

$$R_V = R_1 + R_2 \approx 4.7 \text{ k}$$

$$C \approx 5 \mu\text{F}$$


giving a high time of 0.016 s

frequency of 31.25 Hz \rightarrow 62.5 Hz

a small bias resistor may be needed next to R_2 .

Circuit board layout

Strip-board

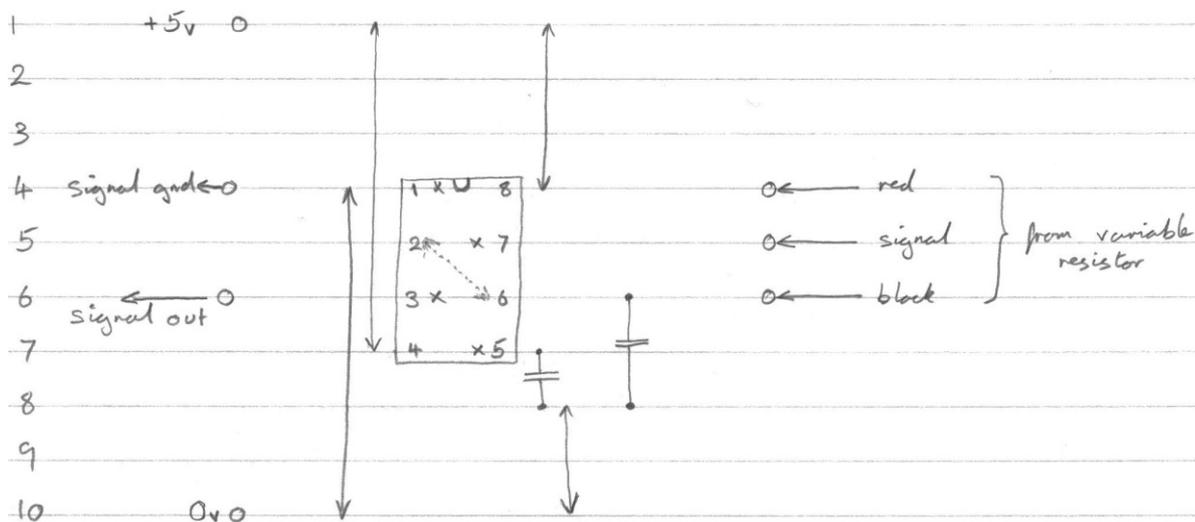


x signifies a cut

+5v may be taken from \overline{INIT} output (pin 16) as long as no more than 4mA is drawn from the point. In this case use,

$$R_i = \frac{5}{4 \times 10^{-3}} \times N \quad \text{where } R_i \text{ is the resistance of each variable resistor and } N \text{ is the number.}$$

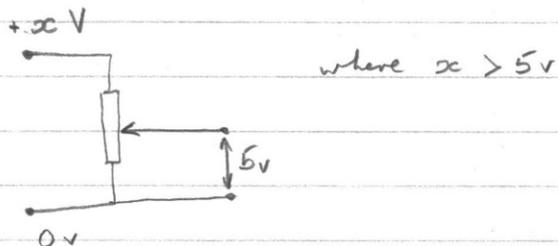A better way to supply power would be to have a separate power supply (eg. from a portable CD player) and use the following circuit to give a 5 volt supply.



The signal outputs are pulses with the high time

$$0.69 (R_1 + R_2) C$$


where R_1 is between pins 7 and 8

R_2 is between pins 6 and 7

C is between pin 6 and ground

Tim Brocklehurst
Marine Design
www.MarineDesign.tk

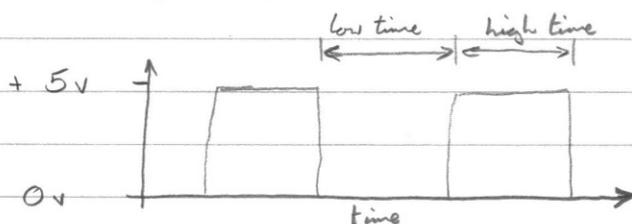
The low time of the pulse is $0.69 R_2 C$



signal output

the position of the variable resistor is derived from the low time by calibration in the computer code.

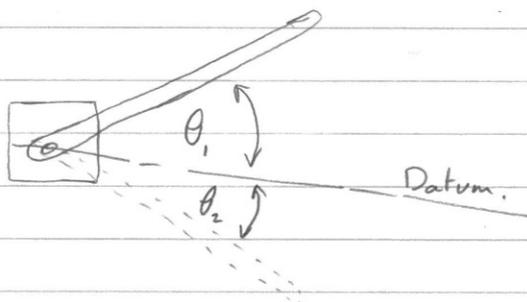Calibration requires the lengths between variable resistors (centres) the offset of the two main arms (from V_{R_1} to the main arm; and the distance between the two arms). All the variable resistors must then be calibrated to at least two angles (say $\pm 45^\circ$ from a datum) the datum should then be cross-checked, i.e.



The following signal out connectors should be used:

$VR_1 \rightarrow D_0$ (pin 2)

$VR_2 \rightarrow D_1$ (pin 3)

$VR_3 \rightarrow D_2$ (pin 4)

$VR_4 \rightarrow D_3$ (pin 5)

$SW_1 \rightarrow D_4$ (pin 6)

Signal gnd / 0v \rightarrow pins 18 \rightarrow 25

Port Locations and Values

Tim Brocklehurst
Marine Design
www.MarineDesign.tk

Data lines = Port + 0

Status lines = Port + 1

Control lines = Port + 2

Typically the port is LPT1 and may be found at an address 888 (or 0x0378 (hex)) this appears to be static between operating systems on standard hardware.

Data lines	value returned
D ₀	1
D ₁	2
D ₂	4
D ₃	8
D ₄	16

if D₁, D₂ and D₃ are high 2+4+8 = 14 will be returned

if used, \overline{INIT} is on port+2 (ie. 890) and has value 4. \overline{INIT} is an output only.

Commands: In C; #include <asm/io.h>

Outb(value, port)

value = inb(port)

In Qbasic; OUT port, value

value = INP(port)

Use these to write to the port. Only use at the beginning of the code to clear the port of data.